

PART B — (5 × 16 = 80 marks)

11. (a) Using Mesh Analysis, find the current through various branches in the circuit of figure 11 a. (16)

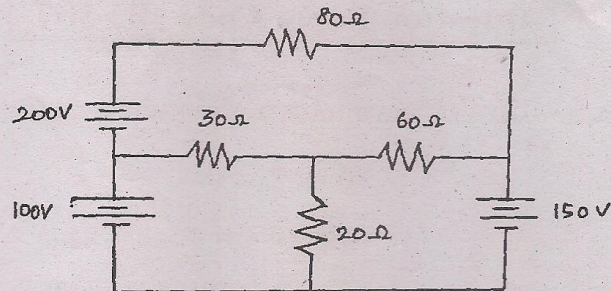


Figure 11 (a)

Or

- (b) Derive the expression for phase angle in the R-L series circuit R-C series circuit and R-L-C series circuit. (16)
12. (a) Explain the construction and working Principle of DC Generator with neat diagram. (16)
- Or
- (b) Explain the working principle of various types of Single Phase (1ϕ) Induction Motor with neat diagram. (16)
13. (a) Explain the working principle of Half wave and Full wave rectifier with neat waveform. (16)
- Or
- (b) Explain various characteristics of BJT in Common Emitter configuration with neat diagram. (16)
14. (a) Explain in detail about D-Flip-Flop, T- Flip-Flop and JK Flip-Flop. (16)
- Or
- (b) Explain working principle of D/A and A/D converters. (16)
15. (a) Explain the Principles of Amplitude Modulation and Frequency Modulation. (16)
- Or
- (b) Explain the configuration of Satellite communication with neat diagram. Give its merits and Demerits. (16)