



Reg. No. : 

|  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |
|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|
|  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |
|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|

**Question Paper Code : 90065**

B.E./B.Tech. DEGREE EXAMINATIONS, NOVEMBER/DECEMBER 2019  
Second Semester  
Mechanical Engineering  
BE 8253 – BASIC ELECTRICAL, ELECTRONICS AND INSTRUMENTATION  
ENGINEERING  
(Common to Aeronautical Engineering/Aerospace Engineering/Automobile  
Engineering/Industrial Engineering/Industrial Engineering and Management/  
Manufacturing Engineering/Marine Engineering/Material Science and  
Engineering/Mechanical Engineering (Sandwich)/Mechanical and Automation  
Engineering/Mechatronics Engineering/Production Engineering/Robotics and  
Automation Engineering)  
(Regulations 2017)

Time : Three Hours

Maximum : 100 Marks

Answer ALL questions

PART – A

(10×2=20 Marks)

1. A stove element draws 15 A when connected to a 120 V line. How long does it take to consume 30 kJ.
2. Write the Mesh equation for the circuit shown in Figure 1.

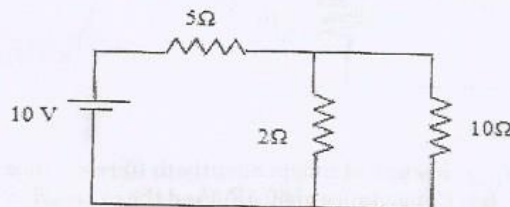


Fig. 1

3. Define Apparent power and power factor.
4. Explain the concept of balanced load.
5. Name the parts of a Transformer.
6. Explain how you would reverse the direction of rotation of a D.C. shunt motor.
7. What is intrinsic semiconductor ?
8. Define the term drift current.

90065

-2-



9. What are the desirable features of a transducer ?
10. List the classifications of instruments.

PART - B

(5×13=65 Marks)

11. a) Using mesh analysis, determine the current through  $1\Omega$  resistor in the given circuit shown in Figure 11.a. (13)

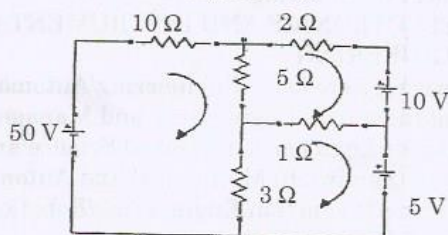


Fig. 11 (a)

(OR)

- b) Find the value of  $R_L$  at which maximum power is transferred to  $R_L$  and hence the maximum power transferred to  $R_L$  in the circuit shown in Figure 11.b. (13)

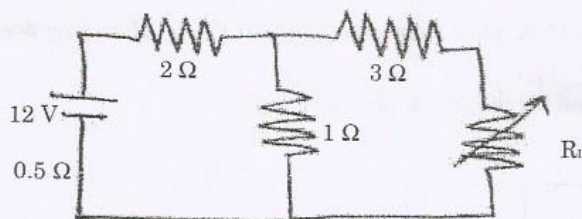


Fig. 11 (b)

12. a) A 50 Hz, A.C. voltage of  $150 V_{(rms)}$  is applied independently to (i) resistance of  $10\Omega$  (ii) Inductance of 0.2 H, (iii) Capacitance of  $50\mu F$ . Find the expression for the instantaneous current and draw the phasor diagram in each case. (13)  
(OR)
- b) Explain three phase circuits in star and delta connection with necessary phasor diagrams and equations. (13)
13. a) Derive the EMF equation of a D.C. generator and explain the working principle of DC generator. (13)  
(OR)
- b) Discuss the principle of operation of a three phase Induction motor. (13)



14. a) Explain the mechanism of avalanche breakdown and zener breakdown. (13)  
(OR)  
b) Discuss using a neat diagram, the principle and working of NPN transistor in CE configuration. (13)
15. a) Explain with a neat sketch, the working of dynamometer type wattmeter. (13)  
(OR)  
b) Explain with necessary diagram, the working principle of a digital storage oscilloscope. Discuss its advantages over analog CRO. (9+4)

PART - C

(1×15=15 Marks)

16. a) Determine the current  $I_L$  in the circuit shown in Figure 16.a.

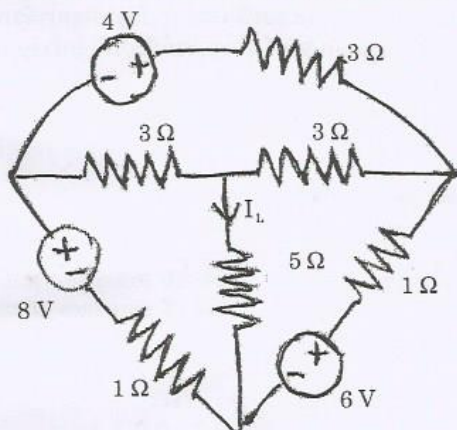


Fig. 16 (a)

(OR)

- b) Determine the current through the 2 ohm resistor in the following network shown in Figure 16. b using Thevenin's theorem.

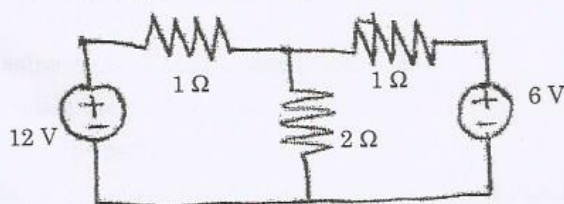


Fig. 16 (b)