

90178

-2-



PART - B

(5×13=65 Marks)

11. a) Simplify the following using Quine Mc-Clusky method.
 $F(A, B, C, D) = \Sigma(0, 1, 2, 3, 5, 7, 8, 10, 12, 13, 15)$ (13)
 (OR)
- b) i) Given $F(A, B, C, D) = \Pi(1, 3, 6, 9, 11, 12, 14)$, draw the K-Map and obtain the simplified expression. (6)
 ii) Simplify and implement $F(A, B, C, D) = \Sigma(0, 4, 8, 9, 10, 11, 12, 14)$ using only NOR-OR logic. (7)
12. a) Explain the operation of BCD to Excess three code Converter. (13)
 (OR)
- b) i) Explain 4-bit magnitude comparator with three outputs: $A > B$, $A = B$ and $A < B$. (8)
 ii) Explain the operation of two bit binary multiplier in detail. (5)
13. a) Design a sequential circuit which has three flip flops A, B and C ; one input X_{in} ; and one output Y_{out} . The state diagram is shown in Figure 1. The circuit is to be designed by treating the unused states as don't care conditions. Analyze the circuit obtain from the design to determine the effect of the unused states. Use D flip flops in the design. (13)

 


Figure 1

(OR)



-3-

90178

- b) i) Design a BCD synchronous counter which counts in the sequence.
0000,0001,0010,0011,0100,0101,0110,0111,1000,1001,0000 (10)
- ii) Discuss the working of 4 bit Johnson Counter with neat diagram. (3)
14. a) An asynchronous sequential circuit is described by the following excitation and output function.
- $$Y = X_1X_2' + (X_1 + X_2')Y, Z = Y.$$
- i) Draw the logic diagram. (3)
- ii) Derive the transition table and output map. (5)
- iii) Describe the behavior of the circuit. (5)
- (OR)
- b) i) Discuss in detail about Races. (6)
- ii) Explain the race free state assignment. (7)
15. a) i) Implement the following using PLA. (6)
- $$F1 = A'B + AC' + A'BC'$$
- $$F2 = (AB + AC + BC)'$$
- ii) Explain TTL log logic family with totem pole output. (7)
- (OR)
- b) i) State the advantages of CMOS logic circuit. (3)
- ii) Explain static RAM cell using MOSFET. (3)
- iii) Write a notes on FPGA with neat diagram. (7)

PART - C

(1×15=15 Marks)

16. a) i) Design an odd parity generator that generates an odd parity bit for every input string of 3 bits. (10)
- ii) Explain the need of Parity Checker circuit with necessary diagrams. (5)

(OR)

www.AllAbtEngg.comAvailable in / AllAbtEngg Android App too,Check www.SmartPoet.Net & www.PhotoShip.Net

90178

-4-



b) Derive the state table and state diagram of the sequential circuit shown in figure. Explain the function that the circuit performs. (15)

